

Logic Diagrams

MUX & Inverters:

This can be turned into a 4:1 MUX!

